

**Pontifícia Universidade Católica de Campinas – PUC
CAMPINAS**

Projeto 2 – CPU

Cesar Marrote Manzano	RA: 18051755
Fabício Silva Cardoso	RA: 18023481
Matheus Henrique Moretti	RA:18082974
Pedro Ignacio Trevisan	RA:18016568

ÍNDICE

1. Descrição textual do projeto com a topologia da CPU
2. Especificação
 - 2.1 Registradores (quantidade, endereço e tamanho)
 - 2.2 Formato das instruções (OPCODE)
 - 2.3 Unidade de Controle: diagrama e tabela de estados, sinais e seus significados
3. Resultados
 - 3.1 Descrição dos testes realizados
 - 3.2 Resultados e discussão
4. Bibliografia, ANEXO


1. DESCRIÇÃO TEXTUAL DO PROJETO COM A TOPOLOGIA DA CPU

O segundo projeto teve como objetivo o desenvolvimento de uma CPU simples, que executa as instruções abaixo:

Instrução	Significado	Descrição
MOV Ri,Rj	$R_i \leftarrow R_j$	Move
MOV Ri,Imed	$R_i \leftarrow \text{Imed}$	Move Immediate
XCHG Ri,Rj	$R_i \leftarrow R_j$ e $R_j \leftarrow R_i$	Exchange
ADD Ri,Rj	$R_i \leftarrow R_i + R_j$	Add
ADDI Ri,Imed	$R_i \leftarrow R_i + \text{Imed}$	Add Immediate
SUB Ri,Rj	$R_i \leftarrow R_i - R_j$	Subtract
SUBI Ri,Imed	$R_i \leftarrow R_i - \text{Imed}$	Subtract Immediate
AND Ri,Rj	$R_i \leftarrow R_i \& R_j$	And
ANDI Ri,Imed	$R_i \leftarrow R_i \& \text{Imed}$	And Immediate
OR Ri,Rj	$R_i \leftarrow R_i R_j$	Or
ORI Ri,Imed	$R_i \leftarrow R_i \text{Imed}$	Or Immediate

Inicialmente, a CPU estará esperando um código válido para que se inicie as operações. Caso exista a necessidade de se fazer uma operação com um imediato, temos um sinal que controla a entrada do dado para o barramento. O barramento (de 8 bits), possui dados circulando para que seja possível realizar as operações necessárias. Os sinais de controle necessitam estar sincronizados com as operações, para não aconteça a perda de nenhum dado, pois usam sempre o mesmo barramento.

Topologia da CPU

 

2. ESPECIFICAÇÃO

2.1. REGISTRADORES (QUANTIDADE, ENDEREÇO E TAMANHO)

Utilizamos quatro registradores principais e três auxiliares. O registrador principal tem como função armazenar os valores para que seja feita as operações. Um dos auxiliares é usado para a instrução XCHG e os outros dois são usados da seguinte forma: um para armazenar o valor que entrará na ULA e outro que conterá o valor da operação da ULA. Todos os 7 registradores possuem tamanho de 8 bits.

2.2 FORMATO DAS INSTRUÇÕES (OPCODE)

INSTRUÇÃO	OPCODE	FORMATO
MOV	0000	-
MOVI	0001	-
XCHG	0010	-
ADDI	0011	TIPO I
SUBI	0100	TIPO I
ANDI	0101	TIPO I
ORI	0110	TIPO I
ADD	0111	TIPO R
SUB	1000	TIPO R
AND	1001	TIPO R
OR	1010	TIPO R

Para podermos testar o programa, adotamos as instruções com 16 bits. Os bits das instruções estão organizados da seguinte forma:

- De 15-12 representam as instruções que serão realizadas, ou seja, irá conter os opcodes;
- De 11-10 representam o registrador destino;
- De 9-8 representam algum registrador temporário;
- De 7-0 representam os imediatos.


2.3. UNIDADE DE CONTROLE: DIAGRAMA E TABELA DE ESTADOS, SINAIS E SEUS SIGNIFICADOS

A tabela abaixo mostra as operações realizadas pela unidade de controle (UC). Cada operação possui o seu respectivo código e quando há códigos inválidos, a UC fica no estado de waiting, ou seja, esperando um código válido para realizar a instrução.

ESTADO	CÓDIGO
MOV	0000

MOVI	0001
XCHG	0010
OPERAÇÕES ARITMETICAS	0011 até 1010
WAITING	Códigos Inválidos

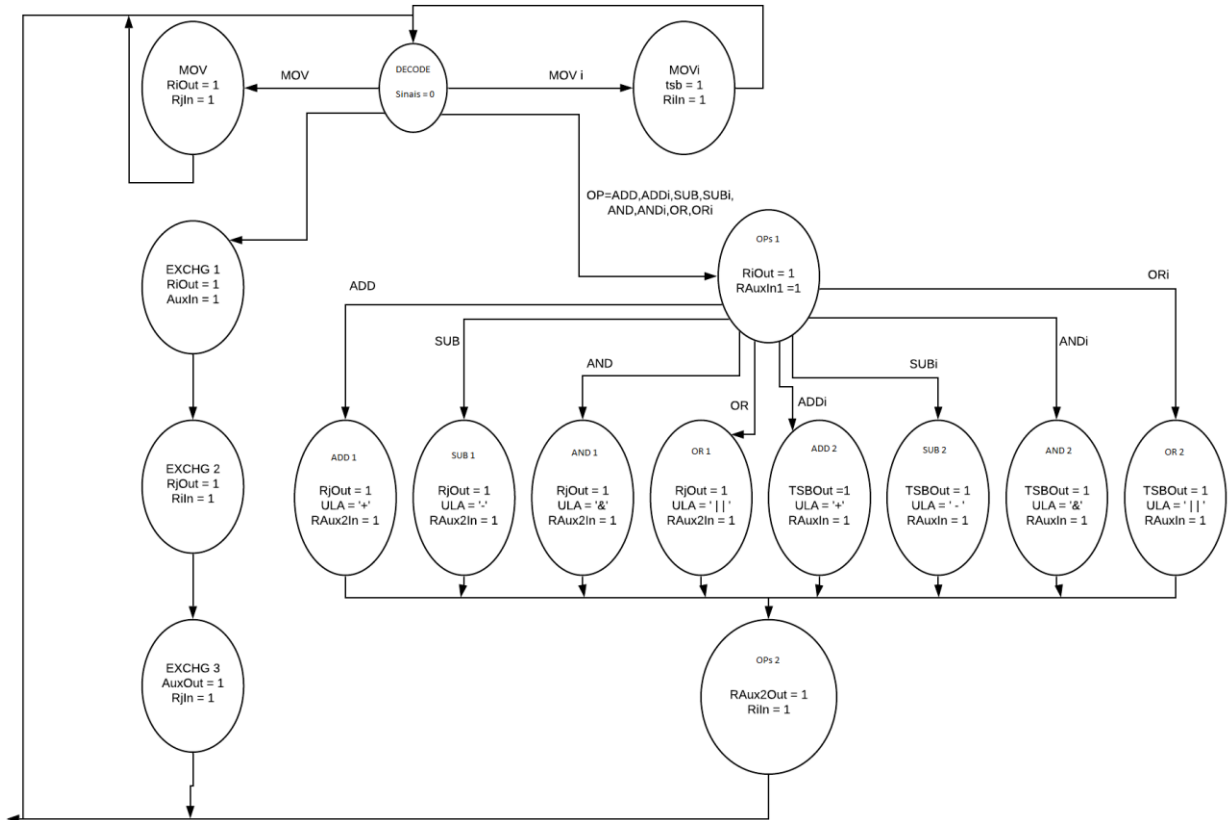O diagrama de estados abaixo representa como será projetada a UC:



3. RESULTADOS



3.1. DESCRIÇÃO DOS TESTES REALIZADOS


Os testes foram realizados na ordem dos opcodes.

INSTRUÇÃO	OPERAÇÃO
0001000000000100	MOVI: REG0 <- 4
0001000000000001	MOVI: REG1 <- 1
0010000010000000	XCHG: REG0 <-> REG1
0101000000000101	ADDI: REG0 <- REG0 ADDI 5
1000110000000011	ORI: REG3 <- REG0 ORI 3
1001000001000000	ADD: REG0 <- REG0 ADD REG1
1010000011000000	SUB: REG0 <- REG3 SUB REG0
0110000000000111	SUBI: REG0 <- REG0 SUBI 7
0000000100000000	MOV: REG0 <- REG1
0111111000001111	ANDI: REG0 <- REG0 ANDI 15

1011111001000000	AND: REG3 <- REG2 AND REG1
1100001000000000	OR: REG0 <- REG2 OR REG0

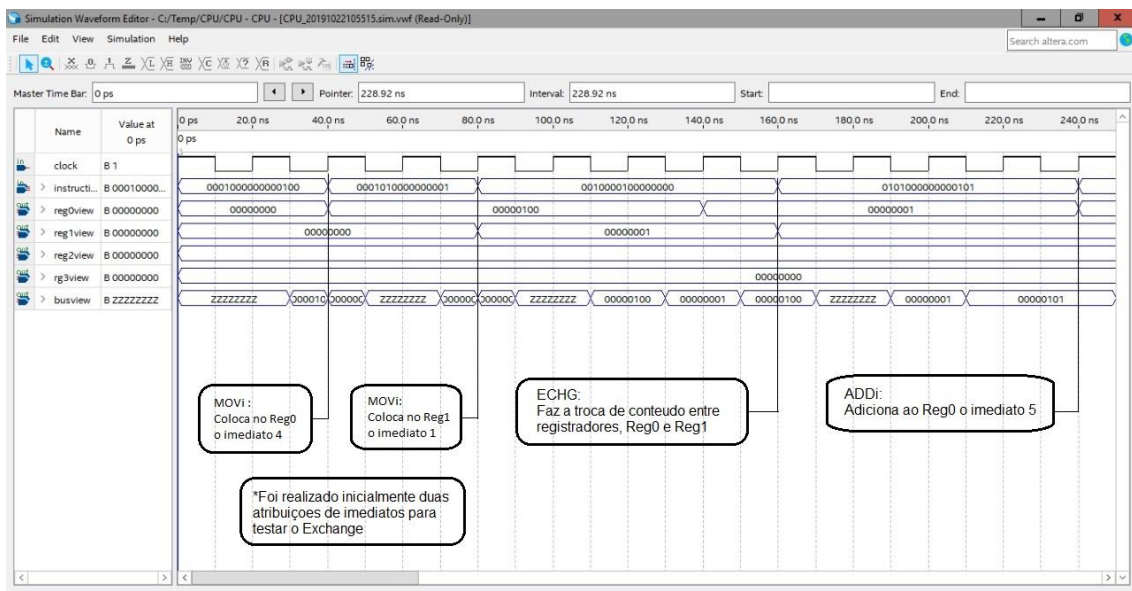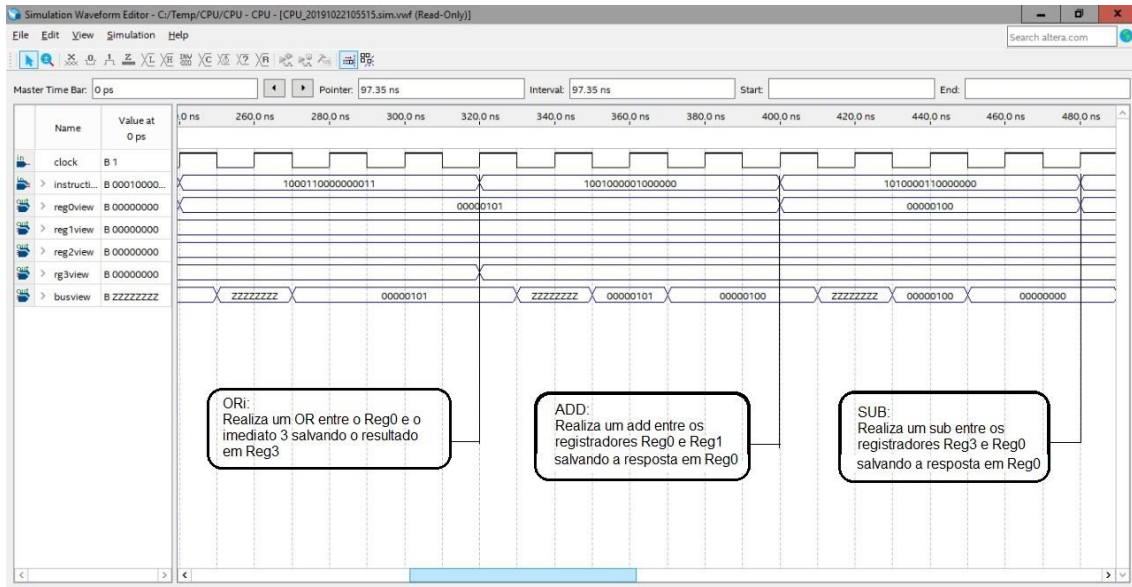As imagens abaixo representam os testes realizados



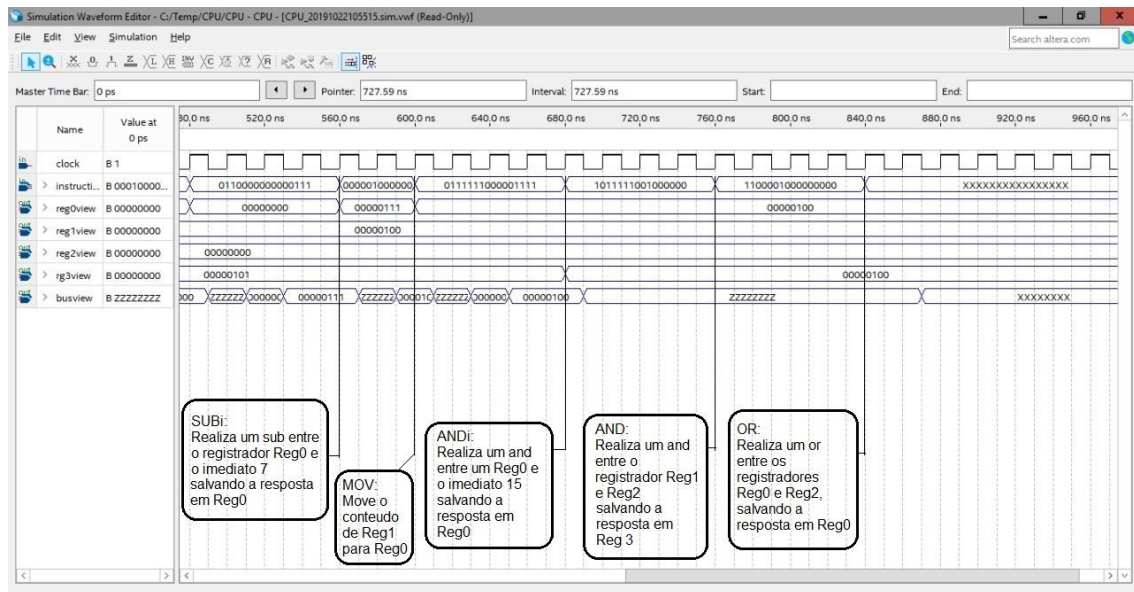

3.2. RESULTADOS E DISCUSSÃO

Todos os testes realizados estão de acordo com o esperado, portanto concluímos que o projeto teve resultado satisfatório.

4. BIBLIOGRAFIA E ANEXO

- Brown S., Vranesic S. "Fundamentals of digital Logic with VHDL Design"

4.1. ANEXO

Código produzido:

ULA.vhd

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.numeric_std.all;

entity ULA is
    port (registrador1: in std_logic_vector(0 to 7);
          registrador2: in std_logic_vector(0 to 7);
          operacao: in std_logic_vector(0 to 1);
          saidaULA: out std_logic_vector(0 to 7));
end ULA;

architecture ALU of ULA is
begin
    process(registrador1, registrador2, operacao)
    begin
        case operacao is
            when "00" => saidaULA <= registrador1 + registrador2;
            when "01" => saidaULA <= registrador1 - registrador2;
            when "10" => saidaULA <= registrador1 and registrador2;
            when "11" => saidaULA <= registrador1 or registrador2;
            when others => saidaULA <= "00000000";
        end case;
    end process;
end ALU;
```


UnidadeControle.vhd

library ieee;

use ieee.std_logic_1164.all;

use ieee.std_logic_unsigned.all;

entity UnidadeControle is

port (instrucao: in std_logic_vector(0 to 15);

clock: in std_logic;

entradaReg0, saidaReg0: out std_logic;

entradaReg1, saidaReg1: out std_logic;

entradaReg2, saidaReg2: out std_logic;

entradaReg3, saidaReg3: out std_logic;

aux1: out std_logic;

entradaAux0, saidaAux0: out std_logic;

entradaAux2, saidaAux2: out std_logic;

imediato: out std_logic;

ALUOp: out std_logic_vector(0 to 1));

end UnidadeControle;

architecture controle of UnidadeControle is

type estadosUC is (esperandoOperacao, mov, movi, xchg, xchg1, xchg2, op0, op1, op2);

signal estado: estadosUC := esperandoOperacao;

signal opcode: std_logic_vector(0 to 3);

signal r1, r2, r3: std_logic_vector(0 to 1);

begin

opcode <= instrucao(0 to 3);

r1 <= instrucao(4 to 5);

r2 <= instrucao(6 to 7);

```

r3 <= instrucao(8 to 9);

process(clock)
begin
if (clock'event and clock = '0') then
    case estado is
        when esperandoOperacao =>
            entradaReg0 <= '0';
            saidaReg0 <= '0';
            entradaReg1 <= '0';
            saidaReg1 <= '0';
            entradaReg2 <= '0';
            saidaReg2 <= '0';
            entradaReg3 <= '0';
            saidaReg3 <= '0';
            aux1 <= '0';
            entradaAux2 <= '0';
            saidaAux2 <= '0';
            entradaAux0 <= '0';
            saidaAux0 <= '0';
            imediato <= '0';
        case opcode is
            when "0000" => estado <= mov;
            when "0001" => estado <= movi;
            when "0010" => estado <= xchg;
            when "0011" => estado <= op0;
            when "0100" => estado <= op0;
            when "0101" => estado <= op0;
            when "0110" => estado <= op0;
            when "0111" => estado <= op0;
            when "1000" => estado <= op0;

```

```

when "1001" => estado <= op0;
when "1010" => estado <= op0;
when others => estado <= esperandoOperacao;
end case;

when mov =>
  case r2 is
    when "00" => saidaReg0 <= '1';
    when "01" => saidaReg1 <= '1';
    when "10" => saidaReg2 <= '1';
    when "11" => saidaReg3 <= '1';
    when others => estado <= esperandoOperacao;
  end case;

  case r1 is
    when "00" => entradaReg0 <= '1';
    when "01" => entradaReg1 <= '1';
    when "10" => entradaReg2 <= '1';
    when "11" => entradaReg3 <= '1';

    when others => estado <= esperandoOperacao;

  end case;

  estado <= esperandoOperacao;

when movi =>
  imediato <= '1';

  case r1 is
    when "00" => entradaReg0 <= '1';
    when "01" => entradaReg1 <= '1';
    when "10" => entradaReg2 <= '1';
    when "11" => entradaReg3 <= '1';
    when others => estado <= esperandoOperacao;
  end case;

```

```

        estado <= esperandoOperacao;
when xchg => -
    entradaAux0 <= '1';
    case r1 is
        when "00" => saidaReg0 <= '1';
        when "01" => saidaReg1 <= '1';
        when "10" => saidaReg2 <= '1';
        when "11" => saidaReg3 <= '1';
        when others => estado <= esperandoOperacao;

    end case;
    estado <= xchg1;
when xchg1 =>
    entradaAux0 <= '0';
    saidaReg0 <= '0';
    saidaReg1 <= '0';
    saidaReg2 <= '0';
    saidaReg3 <= '0';
    case r1 is
        when "00" => entradaReg0 <= '1';
        when "01" => entradaReg1 <= '1';
        when "10" => entradaReg2 <= '1';
        when "11" => entradaReg3 <= '1';

    end case;
    when others => estado <= esperandoOperacao;

    case r2 is
        when "00" => saidaReg0 <= '1';
        when "01" => saidaReg1 <= '1';
        when "10" => saidaReg2 <= '1';
        when "11" => saidaReg3 <= '1';
    end case;

```

```

        when others => estado <= esperandoOperacao;
    end case;

    estado <= xchg2;
when xchg2 =>
    saidaAux0 <= '1';
    case r1 is
        when "00" => entradaReg0 <= '0';
        when "01" => entradaReg1 <= '0';
        when "10" => entradaReg2 <= '0';
        when "11" => entradaReg3 <= '0';
        when others => estado <= esperandoOperacao;
    end case;

    saidaReg0 <= '0';
    saidaReg1 <= '0';
    saidaReg2 <= '0';
    saidaReg3 <= '0';
    case r2 is
        when "00" => entradaReg0 <= '1';
        when "01" => entradaReg1 <= '1';
        when "10" => entradaReg2 <= '1';
        when "11" => entradaReg3 <= '1';
        when others => estado <= esperandoOperacao;
    end case;

    estado <= esperandoOperacao;
when op0 =>
    aux1 <= '1';
    case r2 is
        when "00" => saidaReg0 <= '1';
        when "01" => saidaReg1 <= '1';
        when "10" => saidaReg2 <= '1';

```

```

when "11" => saidaReg3 <= '1';
when others => estado <= esperandoOperacao;
end case;
estado <= op1;
when op1 =>
    aux1 <= '0';
    saidaReg0 <= '0';
    saidaReg1 <= '0';
    saidaReg2 <= '0';
    saidaReg3 <= '0';
    if (opcode > "0110") then
        case r3 is
            when "00" => saidaReg0 <= '1';
            when "01" => saidaReg1 <= '1';
            when "10" => saidaReg2 <= '1';
            when "11" => saidaReg3 <= '1';
            when others => estado <= esperandoOperacao;
        end case;
    else
        imediato <= '1';
    end if;
    case opcode is
        when "0011" => ALUOp <= "00";
        when "0111" => ALUOp <= "00";
        when "0100" => ALUOp <= "01";
        when "1000" => ALUOp <= "01";
        when "0101" => ALUOp <= "10";
        when "1001" => ALUOp <= "10";
        when "0110" => ALUOp <= "11";
        when "1010" => ALUOp <= "11";
    end case;
end when;

```

```

        when others => ALUOp <= "ZZ";
    end case;

    entradaAux2 <= '1';
    estado <= op2;
when op2 =>
    saidaReg0 <= '0';
    saidaReg1 <= '0';
    saidaReg2 <= '0';
    saidaReg3 <= '0';
    entradaAux2 <= '0';
    imediato <= '0';
    case r1 is
        when "00" => entradaReg0 <= '1';
        when "01" => entradaReg1 <= '1';
        when "10" => entradaReg2 <= '1';
        when "11" => entradaReg3 <= '1';
        when others => estado <= esperandoOperacao;
    end case;
    saidaAux2 <= '1';
    estado <= esperandoOperacao;
when others =>
    estado <= esperandoOperacao;
end case;
end if;
end process;
end controle;

```

triStateRegistrador.vhd

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
entity triStateRegistrador is
    port (entradaTR: in std_logic_vector(0 to 7);
          clock: in std_logic;
          enablein: in std_logic;
          enableout: in std_logic;
          reset: in std_logic;
          saidaTR: out std_logic_vector(0 to 7));
end triStateRegistrador;
architecture aux of triStateRegistrador is
    component registrador_8
        port (entradaReg: in std_logic_vector(0 to 7);
              clock: in std_logic;
              enableReg: in std_logic;
              resetReg: in std_logic;
              saidaReg: out std_logic_vector(0 to 7));
    end component;
    component triStateBuffer
        port (entradaTriState: in std_logic_vector(0 to 7);
              controleTriState: in std_logic;
              saidaTriState: out std_logic_vector(0 to 7));
    end component;
    signal med: std_logic_vector(0 to 7);
begin
    reg: registrador_8 port map (entradaTR, clock, enablein, reset, med);
    tri: triStateBuffer port map (med, enableout, saidaTR);
end aux;
```


triStateBuffer.vhd

library ieee;

use ieee.std_logic_1164.all;

use ieee.std_logic_unsigned.all;

entity triStateBuffer is

port (entradaTriState: in std_logic_vector(0 to 7);

controleTriState: in std_logic;

saidaTriState: out std_logic_vector(0 to 7));

end triStateBuffer;

architecture TSB of triStateBuffer is

begin

process(controleTriState, entradaTriState)

begin

if (controleTriState = '1') then

saidaTriState <= entradaTriState;

else

saidaTriState <= "ZZZZZZZZ";

end if;

end process;

end TSB;

registrador 8.vhd

library ieee;

use ieee.std_logic_1164.all;

use ieee.std_logic_unsigned.all;

entity registrador_8 is

port (entradaReg: in std_logic_vector(0 to 7);

clock: in std_logic;

enableReg: in std_logic;

resetReg: in std_logic;

saidaReg: out std_logic_vector(0 to 7));

end registrador_8;

architecture registrador8B of registrador_8 is

begin

process(clock, resetReg)

begin

if (clock'event and clock = '1' and enableReg = '1') then

saidaReg <= entradaReg;

end if;

if (resetReg = '1') then

saidaReg <= "00000000";

end if;

end process;

end registrador8B;

cpu.vhd

library ieee;

use ieee.std_logic_1164.all;

use ieee.std_logic_unsigned.all;

entity cpu is

port(instruction: in std_logic_vector(0 to 15);

clock: in std_logic;

busview: out std_logic_vector(0 to 7);

reg0view: out std_logic_vector(0 to 7);

reg1view: out std_logic_vector(0 to 7);

reg2view: out std_logic_vector(0 to 7);

reg3view: out std_logic_vector(0 to 7));

end cpu;

architecture behavior of cpu is

signal mbus: std_logic_vector(0 to 7);

signal reg0in, reg0out: std_logic;

signal reg1in, reg1out: std_logic;

signal reg2in, reg2out: std_logic;

signal reg3in, reg3out: std_logic;

signal regAin: std_logic;

signal regGin, regGout: std_logic;

signal regTin, regTout: std_logic;

signal imedIn: std_logic;

signal immedi: std_logic_vector(0 to 7);

signal r0insid: std_logic_vector(0 to 7);

signal r1insid: std_logic_vector(0 to 7);

signal r2insid: std_logic_vector(0 to 7);

signal r3insid: std_logic_vector(0 to 7);

```

signal regAtoULA: std_logic_vector(0 to 7);
signal ULAtoRegG: std_logic_vector(0 to 7);
signal ALUOp: std_logic_vector(0 to 1);
signal master_reset: std_logic;

component registrador_8
    port (entradaReg: in std_logic_vector(0 to 7);
          clock: in std_logic;
          enableReg: in std_logic;
          resetReg: in std_logic;
          saidaReg: out std_logic_vector(0 to 7));
end component;

component triStateBuffer
    port (entradaTriState: in std_logic_vector(0 to 7);
          controleTriState: in std_logic;
          saidaTriState: out std_logic_vector(0 to 7));
end component;

component triStateRegistrador
    port (entradaTR: in std_logic_vector(0 to 7);
          clock: in std_logic;
          enablein: in std_logic;
          enableout: in std_logic;
          reset: in std_logic;
          saidaTR
            : out std_logic_vector(0 to 7));
end component;

component ULA
    port (registrador1: in std_logic_vector(0 to 7);
          registrador2: in std_logic_vector(0 to 7);
          operacao: in std_logic_vector(0 to 1);
          saidaULA: out std_logic_vector(0 to 7));

```

end component;

component UnidadeControle

port (instrucao: in std_logic_vector(0 to 15);

clock: in std_logic;

entradaReg0, saidaReg0: out std_logic;

entradaReg1, saidaReg1: out std_logic;

entradaReg2, saidaReg2: out std_logic;

entradaReg3, saidaReg3: out std_logic;

aux1: out std_logic;

entradaAux0, saidaAux0: out std_logic;

entradaAux2, saidaAux2: out std_logic;

imediato: out std_logic;

ALUOp: out std_logic_vector(0 to 1));

end component;

begin

busview <= mbus;

reg0view <= r0insid;

reg1view <= r1insid;

reg2view <= r2insid;

rg3view <= r3insid;

process (instruction)

begin

if (instruction(8) = '0') then

immedi <= instruction(8 to 15);

else

immedi <= instruction(8 to 15);

end if;

end process;

imed: triStateBuffer port map (immedi, imedIn, mbus);

reg0: registrador_8 port map (mbus, clock, reg0in, master_reset, r0insid);

```
tri0: triStateBuffer port map (r0insid, reg0out, mbus);
reg1: registrador_8 port map (mbus, clock, reg1in, master_reset, r1insid);
tri1: triStateBuffer port map (r1insid, reg1out, mbus);
reg2: registrador_8 port map (mbus, clock, reg2in, master_reset, r2insid);
tri2: triStateBuffer port map (r2insid, reg2out, mbus);
reg3: registrador_8 port map (mbus, clock, reg3in, master_reset, r3insid);
tri3: triStateBuffer port map (r3insid, reg3out, mbus);

regA: registrador_8 port map (mbus, clock, regAin, master_reset,
regAtoULA);

regG: triStateRegistrador port map (ULAtoRegG, clock, regGin, regGout,
master_reset, mbus);

regT: triStateRegistrador port map (mbus, clock, regTin, regTout,
master_reset, mbus);

alu: ULA port map (regAtoULA, mbus, ALUOp, ULAtoRegG);

unit: UnidadeControle port map (instruction, clock, reg0in, reg0out,
reg1in, reg1out, reg2in, reg2out, reg3in, reg3out, regAin, regGin, regGout,
regTin, regTout, imedIn, ALUOp);

end behavior;
```